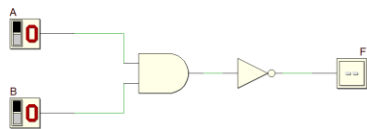


2 Input AND gate

Logic Equation:
 $F = A \cdot B$


Input		Output
A	B	F
0	0	0
1	0	0
0	1	0
1	1	1



2 Input NAND gate

Logic Equation:
 $F = \overline{A \cdot B}$

Input		Output
A	B	F
0	0	1
1	0	1
0	1	1
1	1	0

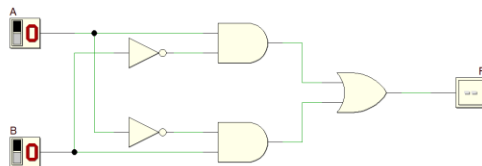

2 Input XOR gate

Logic Equation:
 $F = A \text{ xor } B = A \overline{B} + \overline{A} B$

Input		Output
A	B	F
0	0	0
1	0	1
0	1	1
1	1	0